



Designator	Component	Value
V1	VCC	125V
R1	Resistor	20 Ohms
R2	Resistor	30 Ohms
R3	Resistor	50 Ohms

Schematic	Circuit 1		Create at	2026-05-06
			Update at	2026-05-07
Board			Page	P1
Drawn		Practical Exercise 2 Circuit Design PART B		
Reviewed				
		Version	Size	Page 1 Total 1
EasyEDA		V1.0	A4	EasyEDA.com